

UNIT-3

OSCILLATORS

→ Oscillator is a circuit which generates AC output waveform without any AC input waveform.


→ It generates AC output waveform by making use of DC supply.

Classification of oscillators:



→ There are different classifications.

① Based on output waveform generated:

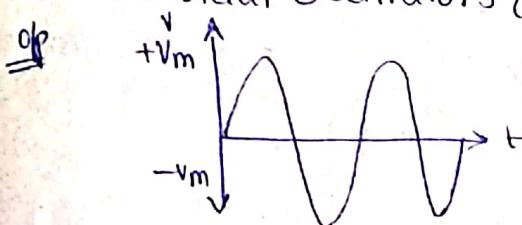ⓐ Sinusoidal Oscillators (or) Harmonic Oscillators.



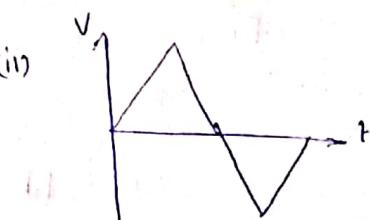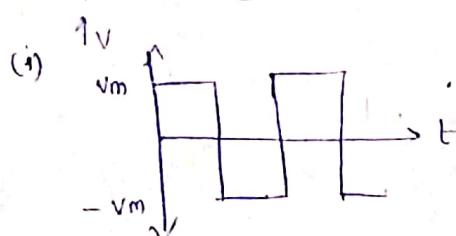ⓑ Relaxation Oscillators (or) Non-sinusoidal oscillators



② Based on fundamental mechanism used:

ⓐ Feedback Oscillator (-ve feedback).

ⓑ Negative Resistance Oscillator eg (BJT, Tunnel diode)

③ Based on frequencies generated:

ⓐ Audio frequency oscillator ($20\text{Hz} - 20\text{kHz}$).

ⓑ Radio frequency oscillator ($20\text{kHz} - 30\text{MHz}$).

ⓒ Very high frequency oscillator ($30\text{MHz} - 300\text{MHz}$).

ⓓ Ultra high frequency oscillator ($300\text{MHz} - 3\text{GHz}$).

ⓔ Microwave frequency oscillator ($> 3\text{GHz}$).

Type of oscillators.

(4) Sinewave oscillators

@ LC oscillators (Simultaneous)

⑥ RC oscillators. (Simultaneous)

10) Condition for sustained oscillations:

$$A_f = \frac{A}{1 - A\beta} \quad (+ve fb)$$

$$\text{if } A\beta = 1 \Rightarrow |A_f| = \infty$$

→ Infinite gain means we can expect some output without any input.

→ Oscillators work on circuit transients and noise.

$$A\beta = 1 \Rightarrow |A\beta| = 1$$

$$A\beta = 1 \text{ rad}^{-1} \cdot 8 \quad \text{LAB} = 0^\circ / 360^\circ$$

↓
Polar form

" $A\beta$ " is loop gain.


Conditions (Barkhausen criterion):—

1) $|A\beta| = 1 \Rightarrow$ Gain around loop must be equal to 1

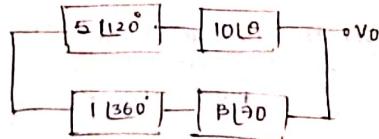2) $\text{LAB} = 0^\circ \text{ or } 360^\circ \Rightarrow$ phase angle around loop must be $0^\circ \text{ or } 360^\circ$.

→ The oscillator circuit is set into oscillations by a random variation caused in the base current due to noise component or a small variation in the dc power supply.

⑦ Calculate θ and β for sustained oscillations.



→ Condition for sustained oscillations,

$$1. |A\beta| = 1$$

$$2. \text{LAB} = 0^\circ$$

1 → Gain around loop (loop gain) must be 1,

$$\Rightarrow 5 \times 10 \times \beta \times 1 = 1$$

$$\Rightarrow \beta = \frac{1}{50}$$

2 → Phase angle around loop must be $0^\circ / 360^\circ$

$$\Rightarrow 120^\circ + 0 + 360^\circ + 70^\circ = 0/360^\circ$$


$$\Rightarrow 0 + 550^\circ = 0/360^\circ$$

$$\Rightarrow 0 + 190^\circ = 0/360^\circ$$

$$\Rightarrow \theta = -190^\circ / 360^\circ$$

practical Considerations for sustained Oscillations:

↳ $|A\beta| > 1$ (Very slightly greater than 1).

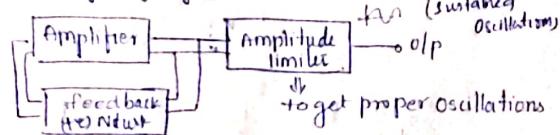

→ Two sin

* Two simple steps to solve any oscillator:

Step-1: Recognize the 'p' network and find 'p'.

$$p = \frac{V_f}{V_0} = (p_{real} + j p_{imaginary}).$$


Step-2: Find Amplifier gain 'A'.

$$A = \frac{V_0}{V_f}$$

$$\text{and } |Ap| = 1. \text{ ie, } A = \frac{V_0}{V_f} [p_{real} + j p_{imaginary}] = 1$$

Separate real and imaginary terms to find out the condition for sustained oscillations.

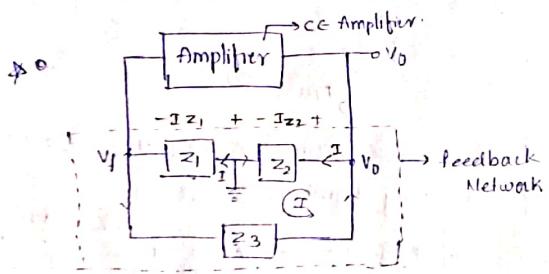General Configuration for LC-Oscillator:-



$$\Rightarrow p = \frac{V_f}{V_0} = -\frac{Iz_1}{Iz_2} = -\frac{z_1}{z_2}$$

$$\hookrightarrow p = -\frac{z_1}{z_2} \quad [-ve sign indicates 180^\circ phase shift]$$

→ Amplifier should also provide $\pm 180^\circ$ since 'p' network is providing 180° phase shift for sustained oscillation.

∴ The amplifier should be CE-Amplifier.

→ In LC Oscillators we have,

(a) Hartley Oscillator (b) Colpitts Oscillator


(a) Hartley Oscillator:

→ If $z_1 = j\omega L_1$, $z_2 = j\omega L_2$ and $z_3 = \frac{1}{j\omega C}$, then it is Hartley oscillator.

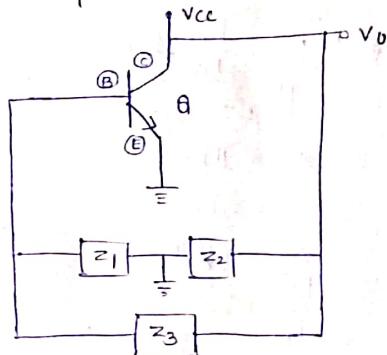(b) Colpitts Oscillator:

→ If $z_1 = \frac{1}{j\omega C_1}$, $z_2 = \frac{1}{j\omega C_2}$ and $z_3 = j\omega L$ then it is colpitts oscillator.

(#) General Configuration of an LC Oscillator with Transistor equivalent circuit :-




* Any of the active devices such as vacuum tubes, FETs, Transistors may be used in amplifier section.

→ z_1, z_2, z_3 are reactive elements constituting the feedback tank circuit which determines f_{osc} .

→ z_1, z_2 serves as an ac voltage divider for o/p voltage & f/fb signal. Voltage across z_1 is f/fb signal.

$$(LC) f_{osc} = \frac{1}{2\pi\sqrt{LC}}$$

→ Ac equivalent circuit:

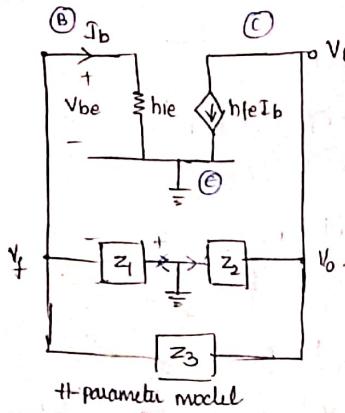

Condition for sustained oscillators:

$$\rightarrow \text{Voltage gain without } h_{fb} \quad A = -\frac{h_{fe}(z_L)}{h_{ie}}.$$

$$z_L = z_2 \parallel (z^1 + z_3)$$

$$\text{where, } z^1 = z_1 \parallel h_{ie}.$$

$$= \frac{z_1 h_{ie}}{z_1 + h_{ie}}$$

$$\Rightarrow z^1 + z_3 = \frac{z_1 h_{ie}}{z_1 + h_{ie}} + z_3.$$

$$\Rightarrow z^1 + z_3 = \frac{z_1 h_{ie} + z_1 z_3 + h_{ie} z_3}{z_1 + h_{ie}}.$$

$$\Rightarrow z^1 + z_3 = \frac{(z_1 + z_3) h_{ie} + z_1 z_3}{z_1 + h_{ie}}$$

$$\therefore \frac{1}{z_L} = \frac{1}{z_2} + \frac{1}{z^1 + z_3}.$$

$$\Rightarrow \frac{1}{z_L} = \frac{1}{z_2} + \frac{z_1 + h_{ie}}{(z_1 + z_3) h_{ie} + z_1 z_3}.$$

$$\Rightarrow \frac{1}{z_L} = \frac{h_{ie}(z_1 + z_2 + z_3) + z_1 z_2 + z_1 z_3}{z_2 [(z_1 + z_3) h_{ie} + z_1 z_3]}.$$

$$\Rightarrow z_L = \frac{z_2 [(z_1 + z_3) h_{ie} + z_1 z_3]}{h_{ie}(z_1 + z_2 + z_3) + z_1 z_2 + z_1 z_3}$$


$$\beta = \frac{V_f}{V_0} \Rightarrow V_f = -\mathcal{I} z^1 \quad (z^1 = z_1 \parallel h_{ie}).$$

$$V_f = \frac{-\mathcal{I} z_1 h_{ie}}{z_1 + h_{ie}}.$$

$$V_0 = -\mathcal{I} (z^1 + z_3)$$

$$= -\mathcal{I} \left[\frac{z_1 h_{ie}}{z_1 + h_{ie}} + z_3 \right]$$
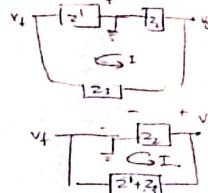
$$= -\mathcal{I} \left[\frac{h_{ie}(z_1 + z_3) + z_1 z_3}{z_1 + h_{ie}} \right].$$



$$\rightarrow \boxed{\beta = \frac{V_f}{V_0} = \frac{z_1 h_{ie}}{h_{ie}(z_1 + z_3) + z_1 z_3}}.$$

$$\Rightarrow \beta \beta_p = 1 \quad (\because \text{for sustained oscillation})$$

$$-\frac{h_{fe}}{h_{ie}} \frac{z_2 [(z_1 + z_3) h_{ie} + z_1 z_3]}{h_{ie}(z_1 + z_2 + z_3) + z_1 z_2 + z_1 z_3} \times \frac{z_1 h_{ie}}{h_{ie}(z_1 + z_3) + z_1 z_3} = 1$$

$$\Rightarrow \frac{-h_{fe} z_1 z_2}{h_{ie}(z_1 + z_2 + z_3) + z_1 z_2 + z_1 z_3} = 1$$

$$\Rightarrow -h_{fe} z_1 z_2 = h_{ie}(z_1 + z_2 + z_3) + z_1 z_2 + z_1 z_3$$

$$\Rightarrow \boxed{h_{ie}(z_1 + z_2 + z_3) + z_1 z_2 [1 + h_{fe}] + z_1 z_3 = 0}$$

Condition for sustained oscillations.


16/01/2020

Heavily Oscillators

For heavily oscillator, $\omega_1 = j\omega L_1 + j\omega M + j\omega(M+L_1)$

$$\omega_2 = j\omega L_2$$

$$\omega_3 = \frac{1}{j\omega C}$$

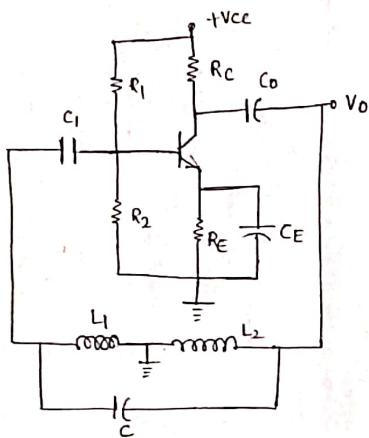

$$\rightarrow h_{fe}(\omega_1 \omega_2 + \omega_3) + \omega_1 \omega_2 (1+h_{fe}) + \omega_1 \omega_3 = 0 \quad \text{--- (1)}$$

from (1)

$$\rightarrow h_{fe} \left[j\omega(L_1 + L_2 + 2M) + \frac{1}{j\omega C} \right] + j^2 \omega^2 \left[L_1 L_2 + M(L_1 + L_2) + M^2 \right] (1+h_{fe}) + j\omega(L_1 + M) \times \frac{1}{j\omega C} = 0$$

$$\rightarrow j\omega h_{fe} \left[(L_1 + L_2 + 2M) - \frac{1}{\omega^2 C} \right] - \omega^2 \left[L_1 L_2 + M(L_1 + L_2) + M^2 \right] (1+h_{fe}) + \left(\frac{L_1 + M}{C} \right) = 0$$

→ equating part on both sides,

$$\Rightarrow j\omega h_{fe} \left[L_1 + L_2 + 2M - \frac{1}{\omega^2 C} \right] = 0$$

$$\omega^2 = \frac{1}{(L_1 + L_2 + 2M)C}$$

$$f = \frac{1}{2\pi\sqrt{(L_1 + L_2 + 2M)C}} \quad (\because \omega = 2\pi f)$$

$$f = \frac{1}{2\pi\sqrt{L_{eq}C}} \rightarrow \text{frequency of oscillations}$$

where, $L_{eq} = L_1 + L_2 + 2M$.

Similarly equating real parts on both sides,

$$-\omega^2 [L_1 L_2 + M(L_1 + L_2) + M^2] [1 + h_{fe}] + \frac{L_1 + M}{C} = 0$$

$$\rightarrow \omega^2 [(L_1 + M)(L_2 + M)] [1 + h_{fe}] = \frac{L_1 + M}{C}$$

$$\rightarrow \frac{1}{(L_1 + L_2 + 2M)C} (L_2 + M)(1 + h_{fe}) = \frac{1}{C}$$


$$1 + h_{fe} = \frac{L_1 + L_2 + 2M}{L_2 + M}$$

$$h_{fe} = \frac{L_1 + M}{L_2 + M} \rightarrow \text{condition for sustainable oscillations in heavily oscillator}$$

$$\text{usually, } h_{fe} \geq \frac{L_1 + M}{L_2 + M}$$

i.e., $(L_1 \geq L_2)$ then only we will get oscillations.

Colpitts Oscillator

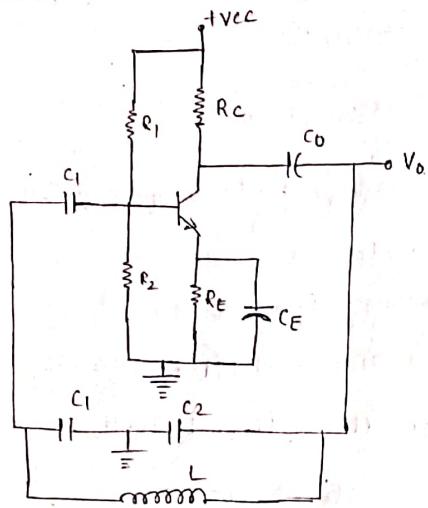

$$\rightarrow z_1 = \frac{1}{j\omega C_1}, \quad z_2 = \frac{1}{j\omega C_2}, \quad z_3 = j\omega L$$

$$\rightarrow h_{ie} (z_1 + z_2 + z_3) + z_1 z_2 (1 + h_{fe}) + z_1 z_3 = 0 \quad \text{---(1)}$$

Sub. z_1, z_2, z_3 in (1),

$$\rightarrow h_{ie} \left[\frac{1}{j\omega} \left(\frac{C_1 C_2}{C_1 + C_2} \right) + j\omega L \right] + \frac{1}{\omega^2 C_1 C_2} (1 + h_{fe}) + \frac{\omega L}{\omega C_1} = 0$$

$$\rightarrow h_{ie} \left[-\frac{j}{\omega} \left(\frac{C_1 C_2}{C_1 + C_2} \right) + j\omega L \right] - \frac{1}{\omega^2 C_1 C_2} (1 + h_{fe}) + \frac{L}{C_1} = 0$$

by taking imag part

$$-\frac{h_{ie}}{\omega} \left(\frac{C_1 C_2}{C_1 + C_2} \right) + h_{ie} \omega L = 0.$$

$$\Rightarrow \frac{h_{ie} (C_1 C_2)}{\omega C_1 C_2} = h_{ie} \omega L$$

$$\Rightarrow \frac{C_1 C_2}{(C_1 + C_2)L} = \omega^2$$

$$\Rightarrow \omega = \frac{1}{\sqrt{L \left(\frac{C_1 C_2}{C_1 + C_2} \right)}}$$

$$\boxed{f = \frac{1}{2\pi \sqrt{L C_{eqv}}}}$$

$$\text{where, } C_{eqv} \Rightarrow \frac{C_1 + C_2}{C_1 C_2} \frac{C_1 C_2}{C_1 + C_2}$$

equating real part,

$$\rightarrow -\frac{1}{\omega^2 C_1 C_2} (1 + h_{fe}) + \frac{L}{C_1} = 0$$

$$\rightarrow \frac{L}{C_1} = \frac{1 + h_{fe}}{\omega^2 C_1 C_2}$$

$$\rightarrow L \omega^2 C_2 = 1 + h_{fe}$$

$$\rightarrow L \left[\frac{1}{\omega^2 \left(\frac{C_1 + C_2}{C_1} \right)} \right] C_2 = 1 + h_{fe}$$

$$\rightarrow \frac{C_1 + C_2}{C_1} = 1 + h_{fe}$$

$$\rightarrow h_{fe} = \frac{C_1 + C_2}{C_1} - 1$$

$$\boxed{h_{fe} = \frac{C_2}{C_1}}$$

$$h_{fe} \geq \frac{C_2}{C_1}$$

27/2/20

Q# In a transistorized Hartley Oscillator two Inductances are 2mH and $20\mu\text{H}$, while the frequency is to be changed from 950kHz to 2050kHz . Calculate range over which the capacitor is to be varied.

→ Given, $L_1 = 2\text{mH}$, $L_2 = 20\mu\text{H}$.

$$L_{eq} = L_1 + L_2 = 2 \times 10^{-3} + 2 \times 10^{-6} \\ = 2.02 \text{mH}$$

$$f_{osc} = \frac{1}{2\pi\sqrt{L_{eq}C}}$$

→ Given, $f_1 = 950\text{kHz} \rightarrow C_1$

$$f_1 = \frac{1}{2\pi\sqrt{L_{eq}C_1}}$$

$$950 \times 10^3 = \frac{1}{2\pi\sqrt{2.02 \times 10^{-3} C_1}}$$

$$C_1 = 13.89\text{pF}$$

→ $f_2 = 2050\text{kHz} \rightarrow C_2$

$$f_2 = \frac{1}{2\pi\sqrt{L_{eq}C_2}}$$

$$2050 \times 10^3 = \frac{1}{2\pi\sqrt{2.02 \times 10^{-3} C_2}}$$

$$C_2 = 2.98\text{pF}$$

→ Range of C from $2.98\text{pF} - 13.89\text{pF}$

Q) Design Colpitts Oscillator for 1MHz frequency.

→ Colpitts Oscillator

$$f_{osc} = \frac{1}{2\pi\sqrt{L_{eq}C}} = 1 \times 10^6 \text{Hz}$$

$$\text{Let } L = 10\mu\text{H}$$

$$1 \times 10^6 = \frac{1}{2\pi\sqrt{10 \times 10^{-6} \times C_{eq}}}$$

$$C_{eq} = 2.53\text{nF}$$


$$C_{eq} = 2.53\text{nF}$$

$$\text{And } C_1 = 5\text{nF} \text{ & } C_2 = 5\text{nF}$$

Q) In a Hartley Oscillator the value of capacitor in a tuned circuit is 500pF and two sections of coil have inductances $38\mu\text{H}$ and $12\mu\text{H}$. Find frequency of oscillations and feedback factor (β)?

$$f_{osc} = \frac{1}{2\pi\sqrt{L_{eq}C}}$$
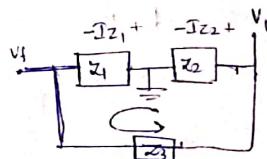
$$\rightarrow L_{eq} = (38 + 12)\mu\text{H} \\ = 50\mu\text{H}$$



$$f_{osc} = \frac{1}{2\pi\sqrt{L_{eq}C}}$$

$$= \frac{1}{2\pi\sqrt{50 \times 10^{-6} \times 500 \times 10^{-12}}} = 1006584.2\text{Hz}$$

$$\approx 1\text{MHz}$$

$$\rightarrow \beta = \frac{V_f}{V_o} = \frac{-I_{Z_1}}{I_{Z_2}} = \frac{-Z_1}{Z_2}$$

$$\rightarrow \beta = -\frac{L_1}{L_2} = -\frac{3.8}{1.2} (\because L_1 > L_2)$$

$$\rightarrow \beta = -3.16$$

$$= 3.16 \angle 180^\circ$$

- (Q) A Colpits Oscillator, the values of inductors & capacitors in a tank circuit are $L = 40 \text{ mH}$, $f_i = 100 \text{ PF}$, $C_2 = 500 \text{ PF}$. Find
 (a) frequency of oscillations (f_{osc})
 (b) if op voltage is 10V. Calculate feedback voltage V_f ?
 (c) Calculate minimum gain if frequency is changed by changing 'L' alone.
 (d) Value of C_1 for a gain of 10. ($h_{fe} = 10$) and also find new frequency (f_{new})?

Sol: $L = 40 \text{ mH}$, $C_1 = 100 \text{ PF}$, $C_2 = 500 \text{ PF}$.

$$f_{osc} = \frac{1}{2\pi\sqrt{LC_{eq}}} = \frac{1}{2\pi\sqrt{40 \times 10^{-3} \times C_{eq}}}$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2} = \frac{100 \times 10^{-12} \times 500 \times 10^{-12}}{(100 + 500) \times 10^{-12}} = 83.3 \text{ PF}$$

$$f_{osc} = \frac{1}{2\pi\sqrt{40 \times 10^{-3} \times 83.3 \times 10^{-12}}}$$

$$= 87.1 \text{ kHz}$$

$$(b) V_0 = 10 \text{ V}, V_f = ?$$

$$\beta = \frac{V_f}{V_0} = -\frac{Z_1}{Z_2} = -\frac{C_2}{C_1}$$

$$\Rightarrow \frac{V_f}{10} = -\frac{500}{100}$$

$$\rightarrow V_f = 50 \text{ V}$$

$$(c) (h_{fe})_{min} = \frac{C_2}{C_1} = \frac{500}{100} = 5$$

$$(d) h_{fe} \cdot 10 = \frac{C_2}{C_1}$$

$$\Rightarrow 10 = \frac{500 \text{ PF}}{C_1}$$

$$C_1 = 50 \text{ PF}$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2} = \frac{50 \times 500}{50 + 500} = 45.45 \text{ PF}$$

$$C_1 = 50 \text{ PF} \quad C_2 = 500 \text{ PF}$$



$$(f_{osc})_{new} = \frac{1}{2\pi\sqrt{L C_{eq}}} = 118.038 \text{ kHz}$$

$$\begin{array}{l} \frac{x}{z} = y \\ z = y \\ m = y \end{array}$$

→ All the oscillators using tuned LC circuits operate well at high frequencies.
At low frequencies as the inductors and capacitors are bulky RC found suitable.

RC phase shift Oscillators (Audio-frequency Oscillators)

(a) 180° (inverting amplifier)

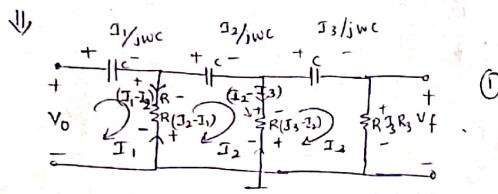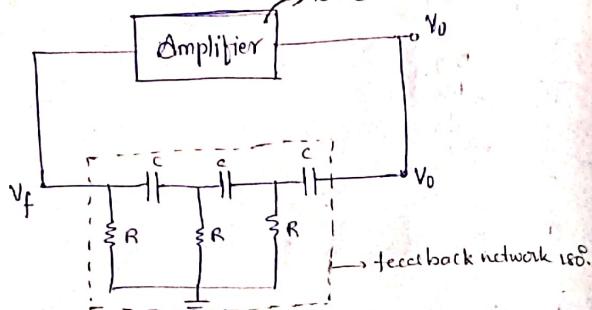

⇒ Applying mesh analysis,

$$KVL(1) \Rightarrow +V_0 - \frac{I_1}{jwC} - R(I_1 - I_2) = 0$$

$$\Rightarrow I_1 \left(R + \frac{1}{jwC} \right) - RI_2 = V_0 \quad (1)$$

KVL(2)


$$\Rightarrow -(I_2 - I_1)R = \frac{I_2}{jwC} - (I_2 - I_3)R = 0$$

$$\Rightarrow -I_1R_1 + I_2 \left(2R + \frac{1}{jwC} \right) - RI_3 = 0 \quad (2)$$

KVL(3)

$$\Rightarrow -(I_3 - I_2)R - \frac{I_3}{jwC} - I_3R = 0$$
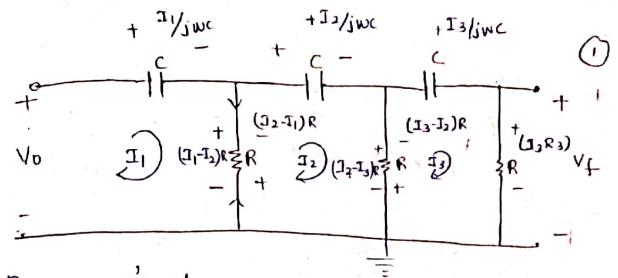
$$\Rightarrow -I_2R + I_3 \left(2R + \frac{1}{jwC} \right) = 0 \quad (3)$$



⇒ By crammer's rule, $I_3 = \frac{D_3}{\Delta}$

$$\Delta = \begin{vmatrix} R + \frac{1}{jwC} & -R & V_0 \\ -R & 2R + \frac{1}{jwC} & 0 \\ 0 & -R & 0 \end{vmatrix}$$

$$\Rightarrow I_3 = 0 - (-R)(0) + V_0(R^2 - 0)$$

$$\left(R + \frac{1}{jwC} \right) \left((2R + \frac{1}{jwC})^2 - R^2 \right) - (-R)((-R)(2R + \frac{1}{jwC}) - 0) + 0$$

$$I_3 = \frac{V_0 R^2}{\left(R + \frac{1}{jwC} \right) \left(4R^2 - \frac{1}{w^2 C^2} + \frac{4R}{jwC} - R^2 \right) - 2R^3 - \frac{R^2}{jwC}}$$

$$= \frac{V_0 R^2}{3R^3 - \frac{R}{w^2 C^2} + \frac{4R^2}{jwC} + \frac{3R^2}{jwC} - \frac{1}{jw^3 C^3} - \frac{4R}{w^2 C^2} - 2R^3 - \frac{R^2}{jwC}}$$

$$= \frac{V_0 R^2}{R^3 - \frac{5R}{w^2 C^2} + \frac{6R^2}{jwC} - \frac{1}{jw^3 C^3}}$$

$$\Rightarrow I_3 = \frac{V_0 R^2}{R^3 \left[1 - \frac{5}{\omega^2 C^2 R^2} + \frac{6}{j \omega R C} - \frac{1}{j \omega^3 C^3 R^3} \right]}.$$

$$B = \frac{V_t}{V_0} = \frac{I_3 R}{V_0}$$

$$= \frac{1}{\left(1 - \frac{5}{\omega^2 C^2 R^2} \right) - j \left[\frac{6}{\omega R C} - \frac{1}{\omega^3 C^3 R^3} \right]}$$

$$\Rightarrow B = \frac{1}{\left(1 - \frac{5}{\omega^2 C^2 R^2} \right) + j \left[\frac{1}{\omega^3 C^3 R^3} - \frac{6}{\omega R C} \right]}.$$

$$\text{Let, } \alpha = \frac{1}{\omega R C}$$

$$\Rightarrow B = \frac{1}{(1 - 5\alpha^2) + j(\alpha^3 - 6\alpha)}.$$

equating imaginary part to zero;

$$\Rightarrow \alpha^3 - 6\alpha = 0$$

$$\alpha^2 = 6$$

$$\alpha = \sqrt{6}$$

$$\Rightarrow \frac{1}{\omega R C} = \sqrt{6}$$

$$\Rightarrow \omega = \frac{1}{\sqrt{6} R C}$$

$$\boxed{f_{\text{osc}} = \frac{1}{2\pi\sqrt{6} R C}}$$

-fosc (freq of oscillations for RC-phaseshift oscillator).

$$\therefore \alpha = \sqrt{6}$$

$$\Rightarrow P = \frac{1}{(1 - 5(\sqrt{6})^2) + j(0)}$$

$$= -\frac{1}{29}$$


$$\Rightarrow P = -\frac{1}{29} \angle 180^\circ //$$

$$\Rightarrow \because AP = 1$$

$$A = \frac{1}{P} = -29$$



$$\Rightarrow A = 29 \angle 180^\circ //$$

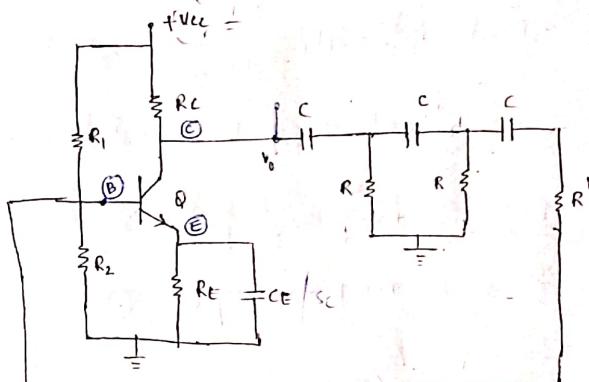RC phase shift Oscillator using BJT (CE):



$$\text{where } R' = R - R_{\text{in}}.$$

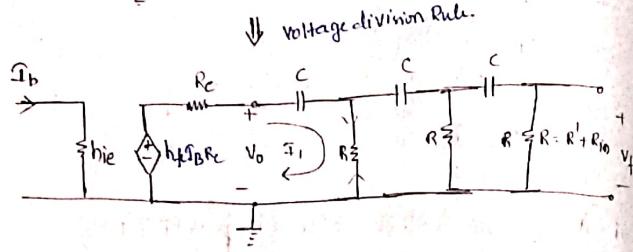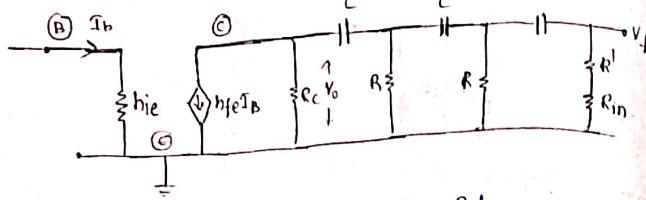→ Draw AC-equivalent Circuit and Replace transistor with h-parameter model.



$$\rightarrow \textcircled{1} \Rightarrow h_{fe}R_C I_b - I_1 R_C - \frac{I_1}{j\omega C} - (I_1 - I_2)R = 0$$

$$\Rightarrow I_1 \left[R_C + R + \frac{1}{j\omega C} \right] - I_2 R = h_{fe}R_C I_b \quad \textcircled{1}$$

$$\textcircled{2} \Rightarrow -I_1 R_1 + I_2 \left[2R + \frac{1}{j\omega C} \right] - I_3 R = 0 \quad \textcircled{2}$$

$$\textcircled{3} \Rightarrow -I_2 R + I_3 \left[2R + \frac{1}{j\omega C} \right] = 0 \quad \textcircled{3}$$

$$I_3 = \Delta_3 / \Delta$$

$$\Rightarrow f_{osc} = \frac{1}{2\pi R C \sqrt{6+4(R_C/R)}}$$

$$f_{osc} = \frac{1}{2\pi R C \sqrt{6+4K}} \quad \text{where } K = \frac{R_C}{R}$$

doubt


$$h_{fe}R_C = -29 - 23K - 4K^2$$

→ condition for sustained oscillations.

$$\rightarrow h_{fe}R_C = \frac{h_{fe}I_b R_C}{I_b} = \frac{V_o}{I_b} = A \quad \beta = h_{fe} = 23129 \frac{R}{R_C} + \frac{4R_C}{R}$$

$$\rightarrow [h_{fe}R_C = A = -29 - 23K - 4K^2]$$

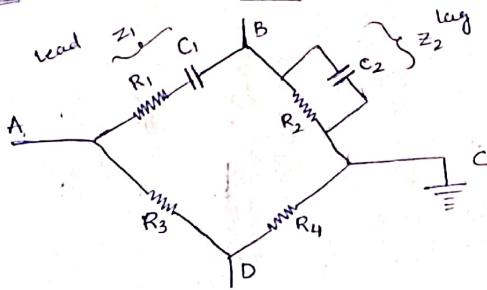WEIN-BRIDGE OSCILLATOR : (lead-lag network)



$$Z_1 = R_1 + \frac{1}{j\omega C_1}$$

$$Z_2 = R_2 \parallel \frac{1}{j\omega C_2}$$


⇒ 'Bridge' is balanced if,

$$\frac{R_3}{R_4} = \frac{Z_1}{Z_2} = \frac{R_1 + \frac{1}{j\omega C_1}}{R_2 \parallel \frac{1}{j\omega C_2}}$$

$$\rightarrow f_{osc} = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$


If $R_1 = R_2 = R$ and $C_1 = C_2 = C$.
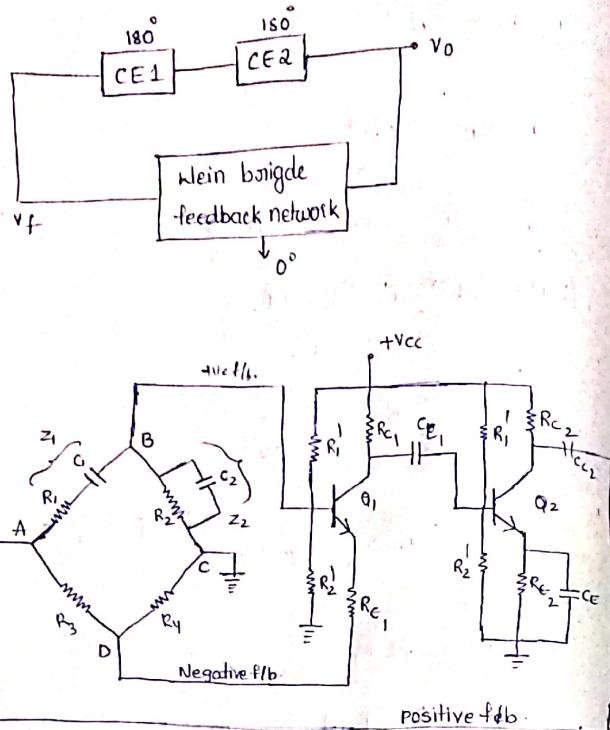
$$\rightarrow f_{osc} = \frac{1}{2\pi R C}$$



- Klein bridge oscillator is used for both negative and positive feedback.
- V_f is measured between point B and C.
- V_0 is measured between point A and C.
- # Feedback network consists of a lead-lag network (R_1-C_1 and R_2-C_2) and a voltage divider (R_3-R_4). The lead-lag network provides a positive feedback to the input of first stage and the voltage divider provides a negative feedback to the emitter of Q_1 .

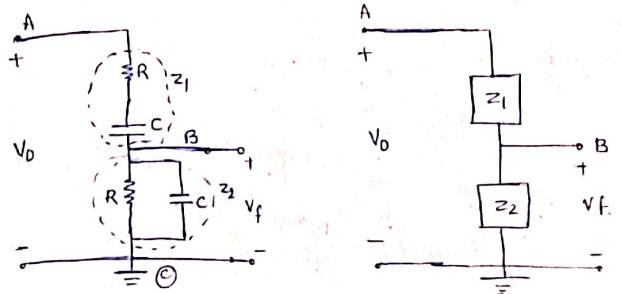Let us consider; $R_1 = R_2 = R$; $C_2 = C_1 = C$.



$$\Rightarrow V_f = \frac{V_0 Z_2}{Z_1 + Z_2}$$

$$\Rightarrow \frac{V_f}{V_0} = \beta = \frac{Z_2}{Z_1 + Z_2}$$

$$\Rightarrow Z_1 = R + \frac{1}{j\omega C}$$

$$Z_2 = R \parallel \frac{1}{j\omega C} \\ = R \left(\frac{1}{j\omega C} \right) \\ \frac{1}{R + \frac{1}{j\omega C}}$$

$$\frac{R/j\omega C}{R + 1/j\omega C}$$

$$R + \frac{1}{j\omega C} + \frac{R/j\omega C}{R + 1/j\omega C}$$

$$\Rightarrow \frac{R}{j\omega RC + 1}$$

$$R + \frac{1}{j\omega C} + \frac{R}{j\omega RC + 1}$$

$$\rightarrow \frac{R}{jWRC + 1}$$

$$\frac{jWRC(jWRC+1) + jWRC + 1 + RjWC}{jWC(jWRC+1)}$$

$$\Rightarrow \frac{jWRC}{-W^2 R^2 C^2 + 3jWRC + 1} / jWRC$$

$$B = \frac{1}{jWRC + 3 + \frac{1}{jWRC}}$$

$$B = \frac{1}{3 + j(WRC - \frac{1}{WRC})}$$

→ To calculate frequency of oscillations make imaginary part of ' B ' equal to zero.

$$\rightarrow WRC - \frac{1}{WRC} = 0$$

$$\omega = 1/RC$$

$$\Rightarrow f_o = \frac{1}{2\pi RC}$$

$$\Rightarrow B = \frac{1}{3+j(0)} \Rightarrow B = \frac{1}{3} 10^\circ$$

$$\rightarrow A\beta = 1 \Rightarrow A = 1/\beta = 3 10^\circ$$

Condition for sustained Oscillations

$$B = \frac{x_2}{x_1 + x_2} = \frac{1}{3}$$

→ If the bridge is balanced,

$$\frac{R_3}{R_4} = \frac{x_1}{x_2}$$

$$\Rightarrow \frac{R_3}{R_4} + 1 = \frac{x_1 + x_2}{x_2} + 1$$

$$\Rightarrow \frac{R_3 + R_4}{R_4} = \frac{x_1 + x_2}{x_2} = 3$$

$$\Rightarrow R_3 + R_4 = 3R_4$$

$$\Rightarrow \boxed{R_3 = 2R_4}$$

Differentiate RC-phase shift Oscillator & Wein Bridge Oscillator.

Rc-phase shift

Wein bridge

1. Consists of 3 identical RC-sections connected in cascade.

2. Feedback network produces 180° phase shift at frequency of oscillations.

3. Amplifier must produce 180° phase shift at freq. of oscillation.

$$4. f_{osc} = \frac{1}{2\pi\sqrt{6}RC}$$

$$5. \beta = -V_{29}$$

6. $|A| \geq 29$ for sustained oscillations.

1. Uses Klein bridge as feedback network.

2. Feedback network produces $0^\circ/360^\circ$ phaseshift at frequency of oscillations.

3. Amplifier must produce $0^\circ/360^\circ$ phaseshift at freq. of oscillation.

$$4. f_{osc} = \frac{1}{2\pi RC}$$

$$5. \beta = V_3$$

6. ~~A ≥ 3~~ $A \geq 3$ for sustained oscillations.

- 7. Inverting amplifier is used.
- 8. Only ^(true) negative feedback is used.
- 9. Relative len stable.
- 10. Cheaper than Kleinbridge
- 11. Non-Inverting amplifier is used.
- 12. Both positive & Negative feeds are used.
- 13. More stable because of negative feedback.
- 14. Costlier than R.C. phase shift oscillator.

* Frequency Stability of an Oscillator

→ Frequency stability of an Oscillator is a measure of its ability to maintain ω nearly a fixed frequency ω possible over as long a time interval as possible.

* Frequency Sensitivity of an oscillator w.r.t temp.

$$S_T = \left[\frac{\Delta \omega}{\omega_0} \right] = \left[\frac{\Delta T}{T_0} \right]$$

where, ω_0 = operating frequency / desired frequency.

T_0 = Operating temperature.

* Frequency stability is given by,

$$S_\omega = \frac{d\phi}{d\omega}$$

change in phase introduced for small change in nominal frequency.


If $\frac{d\phi}{d\omega}$ is more \Rightarrow frequency stability is more.

If D-factor is \uparrow $\frac{d\phi}{d\omega} \uparrow$ stability \uparrow .

To improve frequency stability, i.e., to obtain high degree of frequency stability.

* Crystal Oscillators [using piezo electric crystal].

D

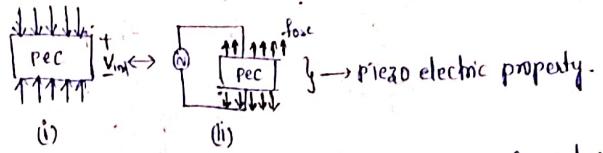

(i) (ii)

(i) When dynamic pressure is applied then voltage is produced.

(ii) When voltage is applied the crystal vibrates.

→ Some of piezo electric materials:

1. Quartz
2. Rochelle salt }
3. Barium Titanate ($BaTiO_3$) } Artificial made.
4. Tourmaline.

→ Vibrating frequency of the crystal is inversely proportional to the thickness of the crystal.

$$f_{osc} = \frac{P}{2l\sqrt{\rho}}$$


where, $P = 1, 2, 3, \dots$

l = thickness of the crystal.

ρ = density of the crystal.


Y = Young's modulus = $\frac{\text{stress}}{\text{strain}}$.

→ Cutting of crystal:

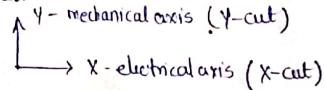

→ Method of manufacturing crystal and thickness decides the vibrating frequency. (T_x thickness).

Circuit symbol of crystal:

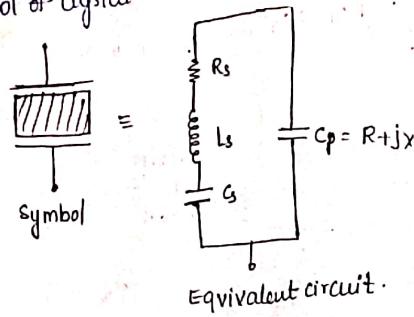

Equivalent circuit.

→ Assume $R_s = 0$;

$$\Rightarrow jX = \left[j\omega C_s + \frac{1}{j\omega C_s} \right] \parallel \left[\frac{1}{j\omega C_p} \right]$$

$$\Rightarrow jX = \frac{1}{j\omega C_p} \left[\frac{\omega^2 - \omega_s^2}{\omega^2 - \omega_p^2} \right]. \quad \omega_s = 2\pi f_s \\ \omega_p = 2\pi f_p$$


where, $f_s = \frac{1}{2\pi\sqrt{L_s C_s}}$ and

$$f_p = \frac{1}{2\pi\sqrt{L_s C_p}} \text{ and } C_{eqv} = \frac{G C_p}{G + C_p}$$

→ f_s : Series Resonant frequency.

f_p : Parallel

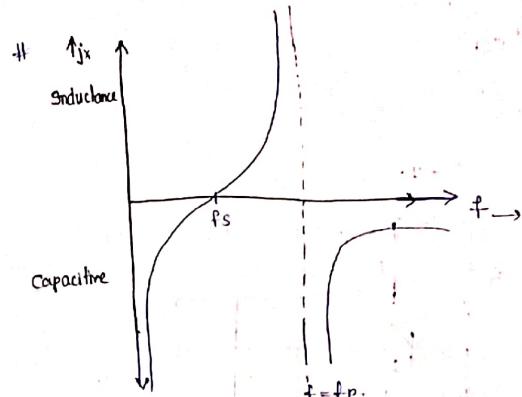
→ If $C_p \gg C_s \Rightarrow C_{eqv} = C_s$ and $f_s = f_p$.



$$Z_L = j\omega L \\ Z_C = \frac{1}{j\omega C} = -\frac{j}{\omega C}$$

Hartley Crystal Oscillator:

→ Replace capacitor with crystal,

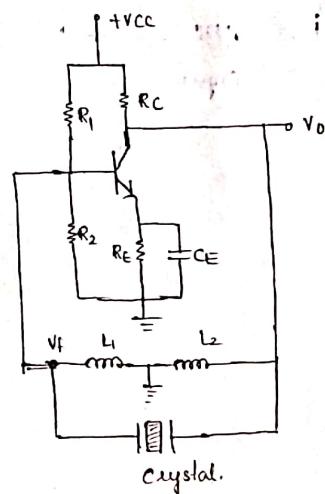

* Colpits Oscillator:

→ Replace Inductor with crystal.

