


## Tuned Amplifiers

→ Tuned amplifiers

- Small signal tuned amplifiers
- Large signal tuned amplifiers

→ To get narrow range of frequencies we use tuned amplifiers.

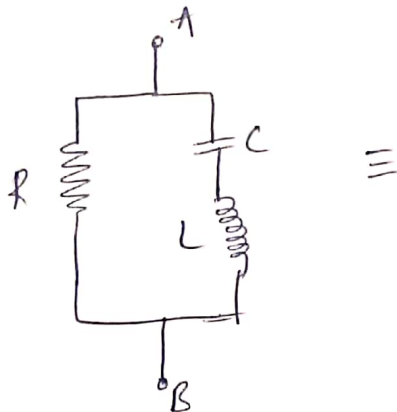→ In tuned amplifiers, a tuned circuit is attached to the collector of the transistor.




Tuned Circuit

At ' $f_0$ ' circuit becomes purely resistive  
( $X_L = X_C$ )


$$\text{Bandwidth} = (f_H - f_L)$$

### Frequency Response:

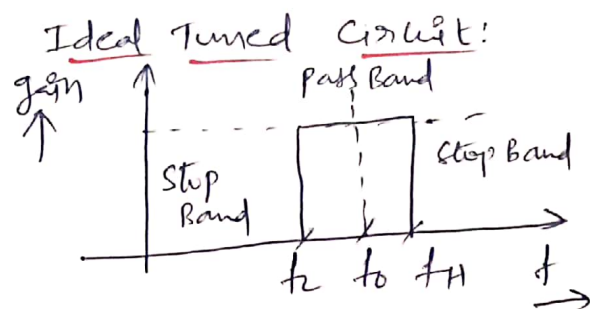
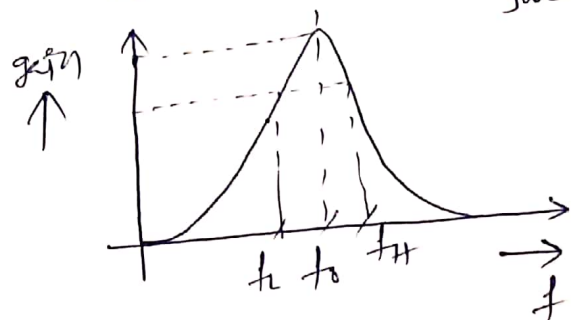
### Practical tuned Circuit:


$$Z_L = R + j\omega L \quad \& \quad Z_C = R + \frac{1}{j\omega C}$$



→ Quality factor: (Q) :- It is defined as

$$Q = 2\pi \times \frac{\text{Maximum Energy stored per cycle}}{\text{Energy dissipated per cycle}}$$

→ For Inductance

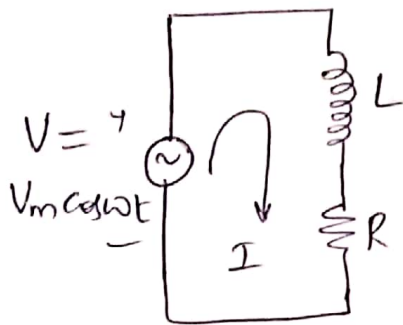

Let  $I_m \rightarrow$  Peak value of current 'I', then

→ Max. Energy stored in inductor per

Cycle is  $E_{\max} = \frac{1}{2} L I_m^2$

→  $P = V \cdot I$  &  $V = L \frac{dI}{dt}$

$\Rightarrow P = L \cdot I \cdot \frac{dI}{dt}$

→  $E = \int P \cdot dt = \int \left[ L \cdot I \cdot \frac{dI}{dt} \right] dt$

$\Rightarrow E_{\max} = \frac{1}{2} L I_m^2$

→ Average power dissipated per cycle

$P = I_{\text{rms}}^2 \cdot R = \left( \frac{I_m}{\sqrt{2}} \right)^2 \cdot R = \frac{I_m^2 R}{2}$

→ Energy dissipated per cycle (E) =  $P \times T$

$= \frac{I_m^2 R}{2} \cdot \frac{1}{f}$


→  $Q = 2\pi \times \frac{\frac{1}{2} L \cdot I_m^2}{\frac{I_m^2 R}{2} \cdot \frac{1}{f}} = \frac{2\pi f \cdot L}{R}$

$\Rightarrow \boxed{Q = \frac{\omega L}{R}}$

→ If inductor is pure  $\Rightarrow R = 0$

$\Rightarrow \boxed{Q = \infty}$

→ For Capacitor:-

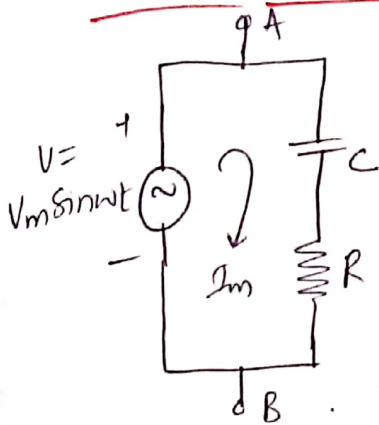

$$\rightarrow E_{\max} = \frac{1}{2} C V_{\max}^2$$

( $V_{\max} \neq V_m$ )

$$\rightarrow V_{\max} = I_m \left[ \frac{1}{\omega C} + R \right]$$

$$\text{If } \frac{1}{\omega C} \gg R \Rightarrow V = V_{\max}$$

$$\Rightarrow V_{\max} = \frac{I_m}{\omega C}$$

$$\left\{ \begin{array}{l} P = V \cdot I \\ = C \cdot V \cdot \frac{dV}{dt} \\ E = \int P \cdot dt \end{array} \right.$$

$$\Rightarrow E_{\max} = \frac{1}{2} C \cdot \frac{I_m^2}{\omega^2 C^2} = \frac{1}{2} \frac{I_m^2}{\omega^2 C}$$


$$\rightarrow E_{\text{dissipated}} = \frac{1}{2} I_m^2 \cdot \frac{R}{f}$$

$$\rightarrow Q = 2\pi \cdot \frac{\frac{1}{2} \frac{I_m^2}{\omega^2 C}}{\frac{1}{2} I_m^2 \cdot \frac{R}{f}} = \frac{2\pi f}{\omega^2 C R} = \frac{\omega}{\omega^2 C R}$$

$$\Rightarrow Q = \frac{1}{\omega R C}$$

$$\rightarrow \text{If } R=0 \Rightarrow Q = \infty \leftarrow \text{For pure Capacitor.}$$

→ For lossy Capacitor

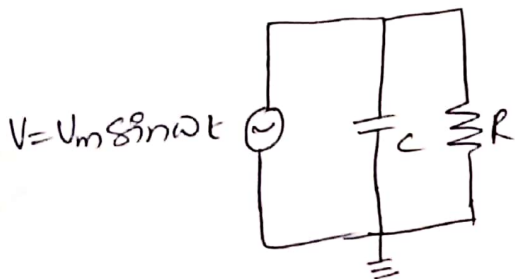

$$E_{\max} = \frac{1}{2} C V_m^2 \quad (\because V_{\max} = V_m)$$

$$E_{\text{dissipated}} = \frac{V_m^2}{2} \cdot \frac{1}{R \cdot f}$$

$$Q = \frac{2\pi \times \frac{1}{2} C V_m^2}{\frac{V_m^2}{2} \cdot \frac{1}{R f}}$$

$$\Rightarrow Q = \omega R C$$

→ loaded and Unloaded (Q) :-

- Unloaded (Q): No load is connected to the tank circuit

$$Q_{\text{unloaded}} = 2\pi \times \frac{\text{Max. Energy stored per cycle}}{\text{Energy dissipated per cycle}}$$

- loaded (Q) :-

$$Q_{\text{loaded}} = 2\pi \times \frac{\text{Max. Energy stored per cycle}}{\left[ \text{Energy dissipated per cycle} \right] + \left[ \text{Energy dissipated due to the presence of external load} \right]}$$

→ Bandwidth decreases as Q-factor increases

↳ selectivity ~~decreases~~ increases

$$\boxed{BW = \frac{f_r}{Q}}$$


→ BW = Bandwidth

$f_r$  = Resonant frequency of the tuned circuit

## → Small Signal Tuned amplifiers:-

- Single tuned amplifiers
  - Capacitor Coupled
  - Inductor Coupled
- Double tuned amplifiers
- Stagger tuned amplifiers.
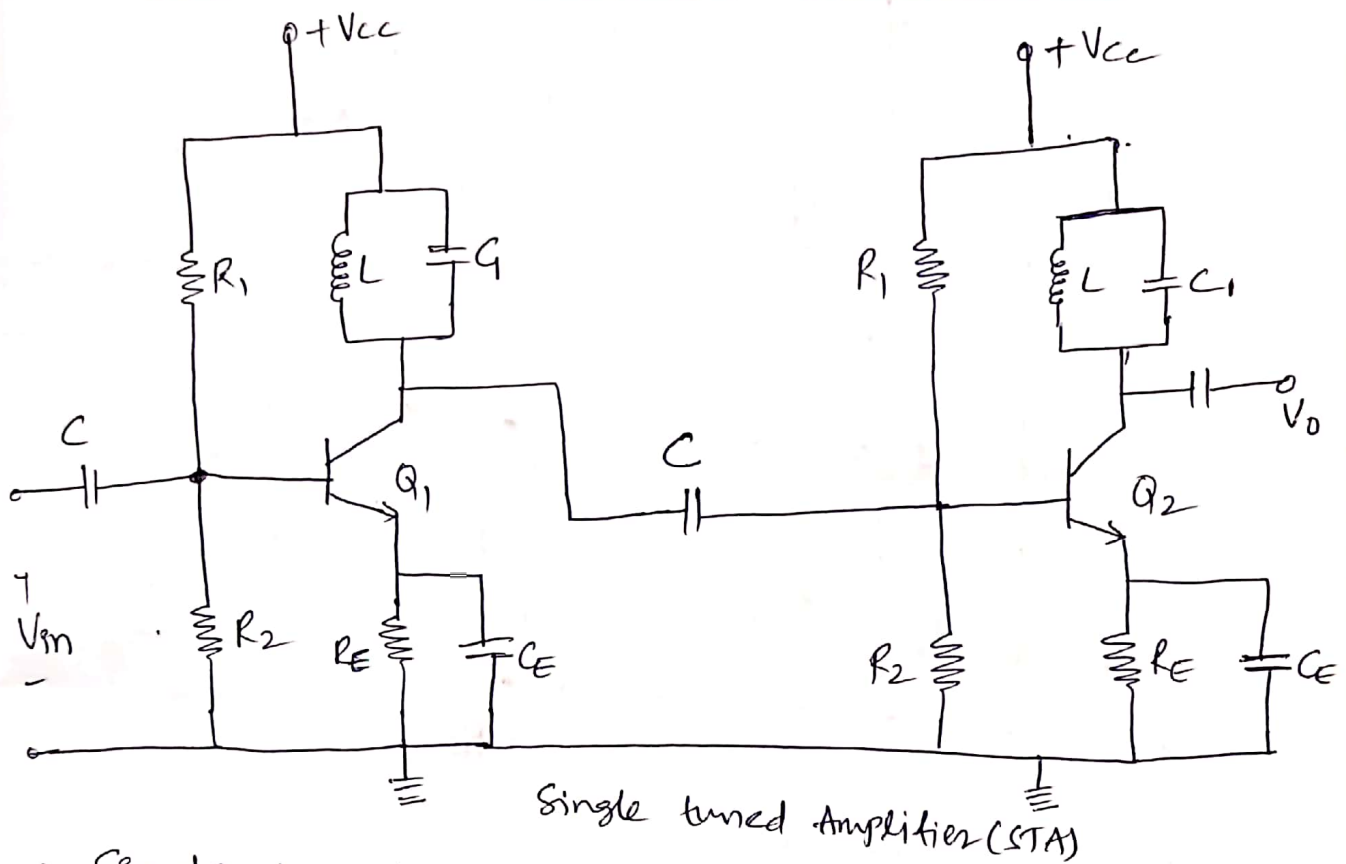
## → Capacitor Coupled Single tuned amplifiers:-




- Single tuned amplifiers use one parallel resonant circuit as load impedance in each stage and all the tuned circuits are tuned to the same frequency.
- Double tuned amplifiers use two inductively coupled tuned circuits per stage, both the tuned circuits being tuned to the same frequency.




→ stagger tuned amplifiers use a number of single tuned stages in cascade, the successive tuned circuits being tuned to slightly different frequencies.

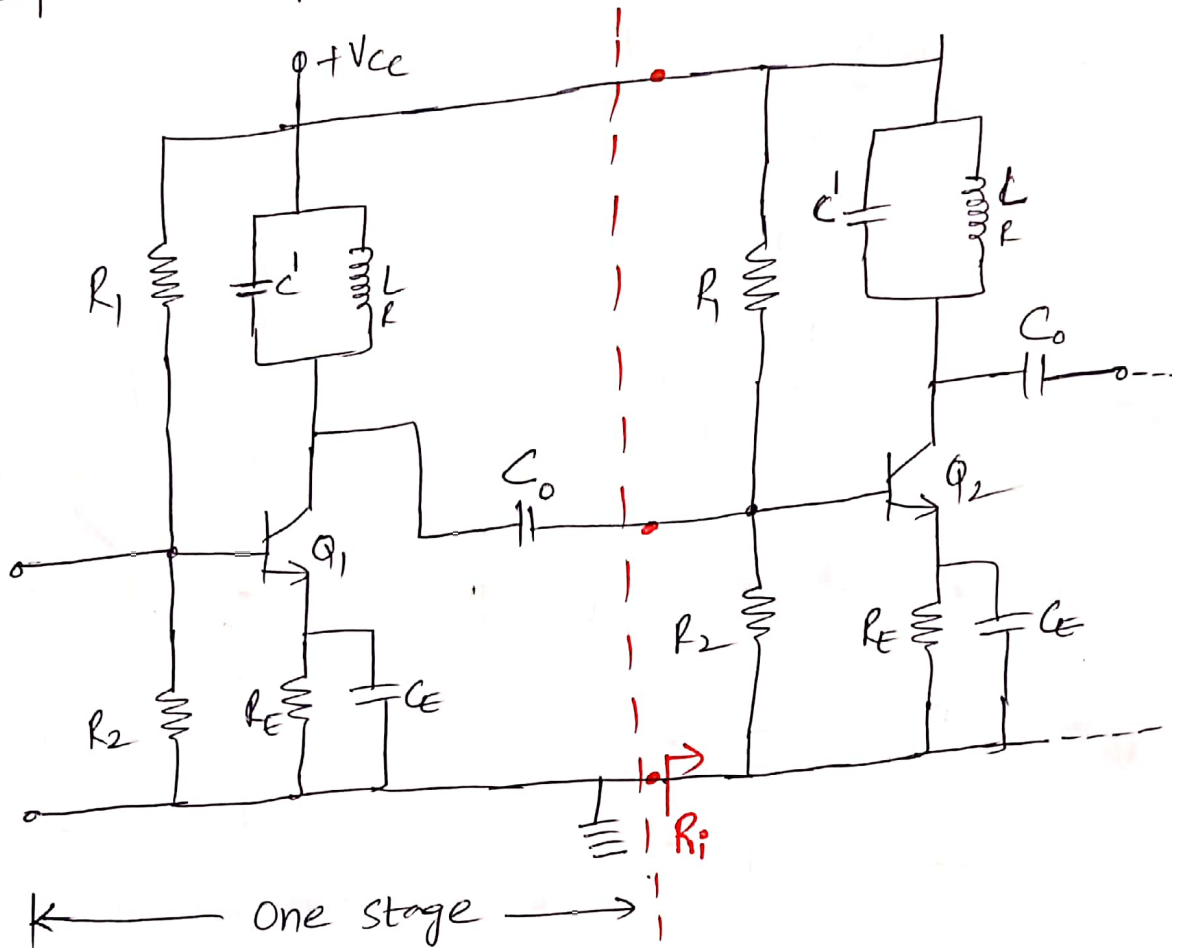→ Capacitor coupled single tuned Amplifier:-



AC Analysis:- (Using high-frequency  $\pi$  model):-


↳ Consider one stage.

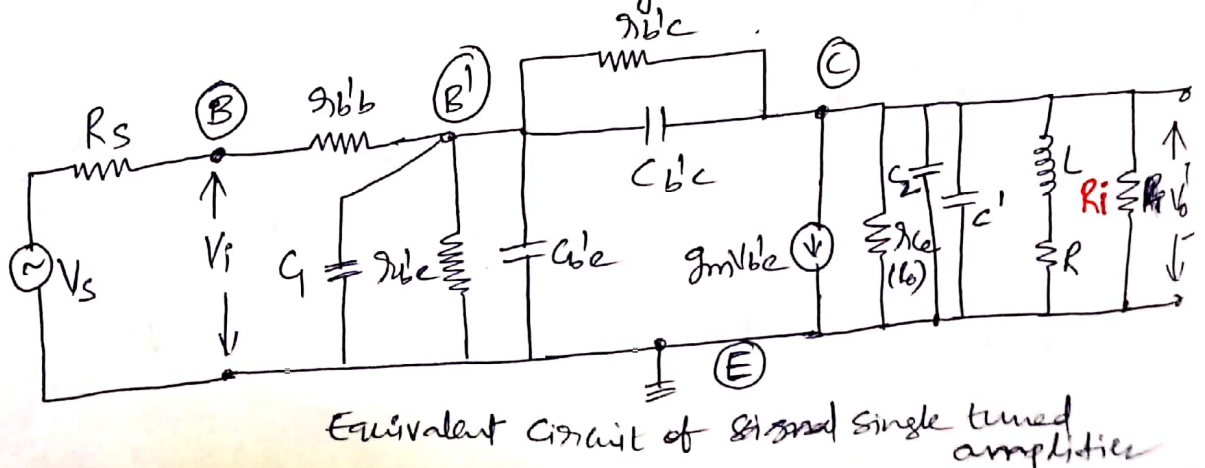

→ Where

- $R_i$  : is the input resistance of the next stage .
- $C_{be}$  are stray wiring capacitances at i/p & o/p ports .  
respectively


→ Miller's Theorem -

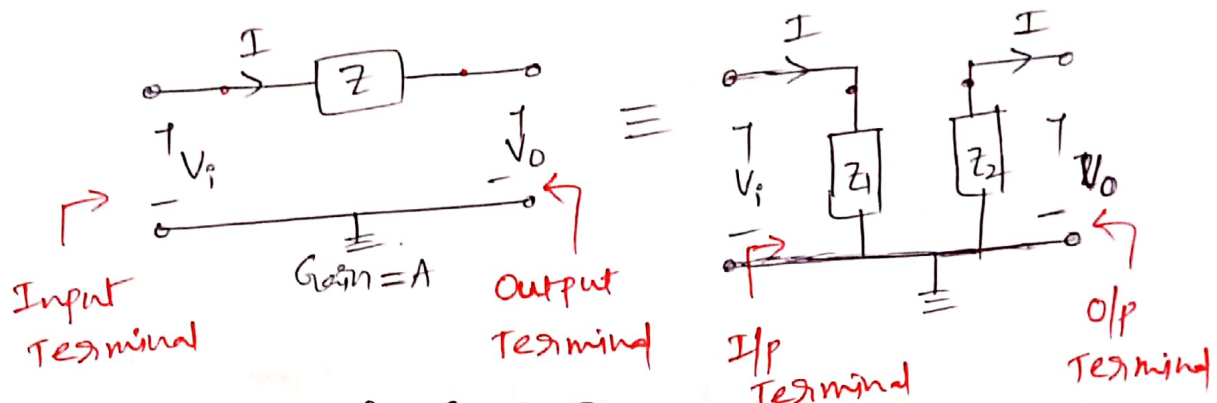

→ In an amplifier circuit with gain 'A',  
An impedance 'Z' connected between input and output  
terminals can be distributed to input and  
output terminals separately as  $Z_1$  and  $Z_2$


where  $Z_1 = \frac{Z}{(1-A)}$  and  $Z_2 = Z \left( \frac{A}{A-1} \right)$

Proof:

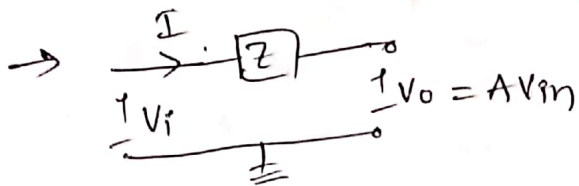

$$I = \frac{V_i - V_o}{Z} = \frac{V_i - AV_i}{Z}$$

$$\Rightarrow I = \frac{V_i (1-A)}{Z}$$

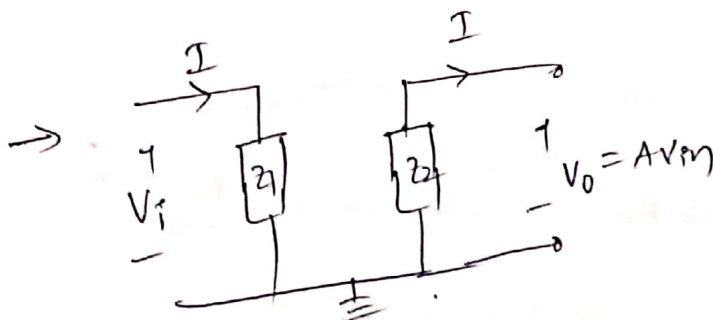

→ At input terminal

$$I = \frac{V_i - 0}{Z_1} \Rightarrow V_i = Z_1 I = \frac{V_i Z}{V_i (1-A)}$$

$$\Rightarrow Z_1 = \frac{Z}{(1-A)}$$

→ At output terminal


$$\rightarrow I = \frac{0 - V_o}{Z_2} \Rightarrow Z_2 = -\frac{V_o}{I}$$

$$\Rightarrow Z_2 = -\frac{AV_i}{I} \quad (\because V_o = AV_i)$$

$$= -\frac{AV_i}{\frac{V_i(1-A)}{Z}}$$

$$\Rightarrow \boxed{Z_2 = \frac{ZA}{(A-1)}}$$

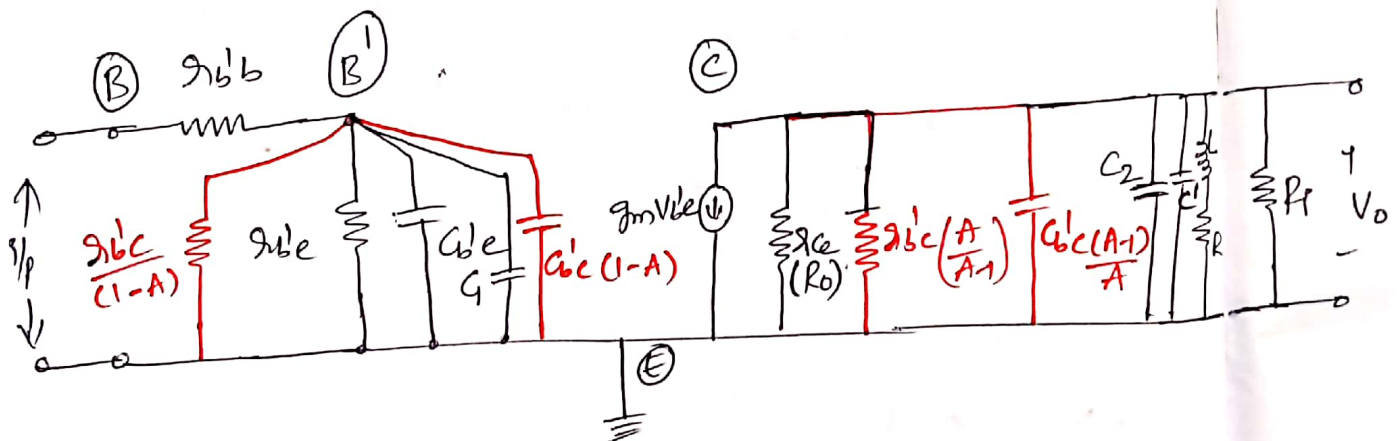→ Applying Miller's theorem to the equivalent circuit of single tuned amplifiers.



Where  $A$  is the amplifier gain &  $A \gg 1$

and  $r_{ce} = R_o$

At output side:

$$\rightarrow \because A \gg 1 \Rightarrow r_{bc} \left( \frac{A}{A-1} \right) = r_{bc}$$

$$\text{and } r_{bc} \gg R_o \Rightarrow \boxed{r_{bc} \parallel R_o \simeq R_o} \Rightarrow \boxed{\text{Neglect } r_{bc}}$$

( $r_{bc}$  is the reverse biased resistance of the junction  $J_c$ )



Let  
 $\rightarrow C_m = C_b'c(1-A) + C_1 + C_{be}$

$\rightarrow C = C' + C_b'c \frac{(A-1)}{A} + C_2$

$\rightarrow$  At the input side

$\frac{r_{bc}}{(1-A)} \gg r_{be}$   
 $\hookrightarrow$  Forward resistance of junction ' $J_E$ '

$\Rightarrow \left[ \frac{r_{bc}}{(1-A)} \parallel r_{be} \right] \approx r_{be}$


$\Rightarrow$  Neglect  $\frac{r_{bc}}{(1-A)}$

$\rightarrow$  Input time constant is much less than

output time constant


$\therefore C_m$  is neglected.

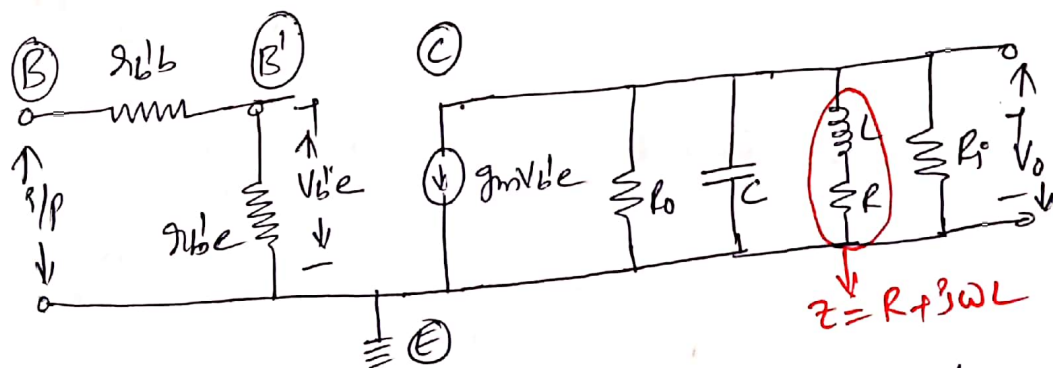$\rightarrow$  (Time Constant  $\neq R'_{bc}$ )  
 $= RC$



Simplified equivalent circuit of single tuned amplifier.

$\rightarrow$  Consider

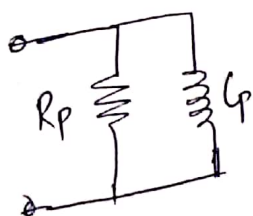

$\frac{1}{Z} = \frac{1}{R_p} + \frac{1}{C_p} = Y$

$\Rightarrow Y = \frac{1}{R_p} + \frac{1}{C_p}$

→ From the simplified equivalent circuit

$$Z = R + j\omega L$$

$$\Rightarrow Y = \frac{1}{R + j\omega L} = \frac{R - j\omega L}{R^2 + \omega^2 L^2}$$

$$\Rightarrow Y = \frac{R}{R^2 + \omega^2 L^2} - \frac{j\omega L}{R^2 + \omega^2 L^2}$$

Comparing with  $Y = \frac{1}{R_p} + \frac{1}{j\omega L_p}$

$$R_p = \frac{R^2 + \omega^2 L^2}{R}, \quad L_p = \frac{R^2 + \omega^2 L^2}{\omega^2 L}$$

→ ~~Redrawing~~

Let  $Q_0$  be the Q-factor at resonance given by

$$Q_0 = \frac{\omega_0 L}{R} \quad \because \omega L \gg R$$

$$\Rightarrow \frac{\omega L}{R} \gg 1 \quad \left| \quad \frac{R}{\omega L} \ll 1 \right|$$


$$\Rightarrow R_p = \frac{R^2 + \omega^2 L^2}{R} = R + \frac{\omega^2 L^2}{R}$$

$$\Rightarrow \boxed{R_p \approx \frac{\omega^2 L^2}{R}} \quad (\because \frac{\omega L}{R} \gg 1)$$


$$\Rightarrow L_p = \frac{R^2 + \omega^2 L^2}{\omega^2 L} = \frac{R^2}{\omega^2 L} + L$$

$$\Rightarrow \boxed{L_p \approx L} \quad (\because \frac{R}{\omega L} \ll 1)$$

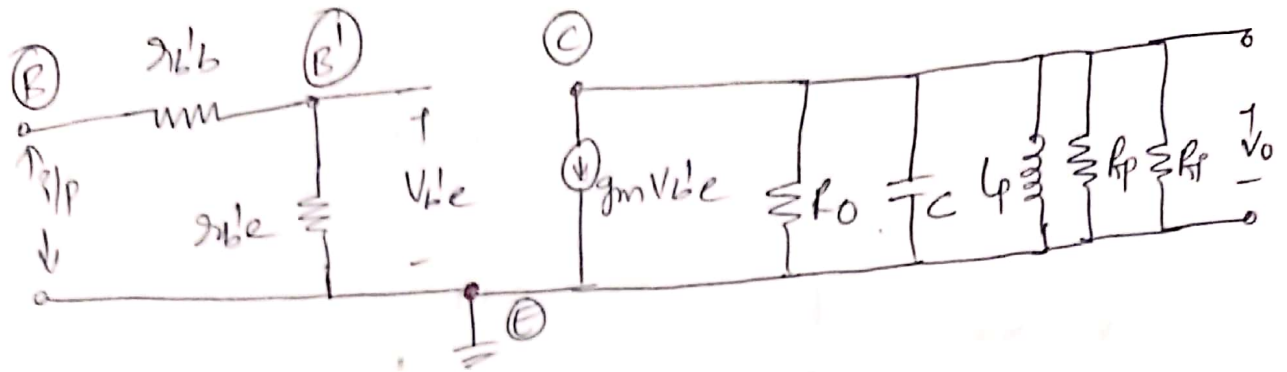→ Re-drawing simplified equivalent circuit



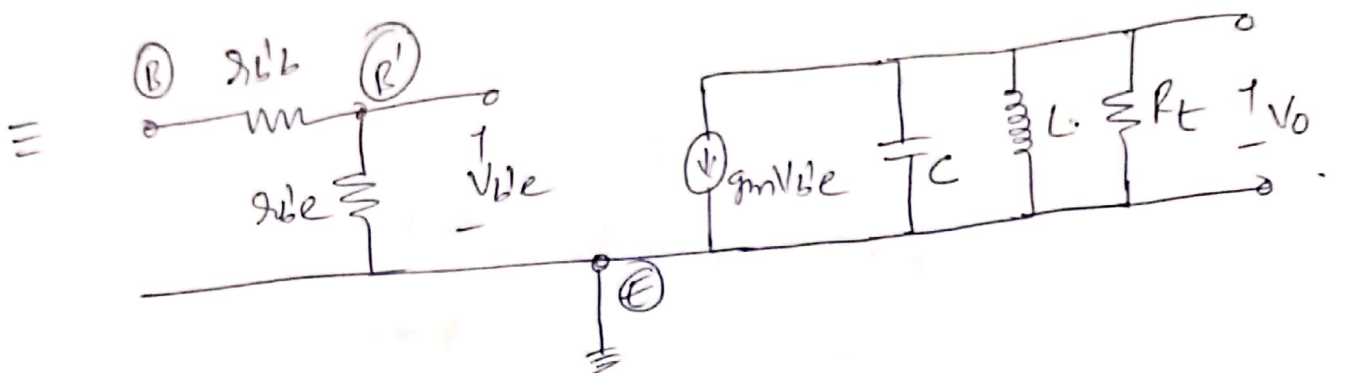Let  $R_o \parallel R_f \parallel R_L = R_t$



Q-factor

The effective Q-factor of the entire output circuit at resonant frequency ' $\omega_0$ ' is given by

$$Q_e = \frac{\text{Susceptance of the inductor (L) (or) Capacitor (C)}}{\text{Conductance of resistance (R)}}$$

Notes Conductance =  $\frac{1}{\text{Resistance}}$  , Susceptance =  $\frac{1}{\text{Reactance}}$

$$\text{Admittance} = \frac{1}{\text{impedance}}$$

$$\& \text{ Impedance} = \text{Resistance} + j (\text{Reactance})$$

$$\text{Admittance} = \text{Conductance} + j (\text{Susceptance})$$

$$\therefore Q_{e(L)} = \frac{1/\omega_0 L}{1/R_t} = \frac{R_t}{\omega_0 L}$$

$$Q_{e(C)} = \frac{\omega_0 C}{1/R_t} = \omega_0 C R_t$$

$$\Rightarrow \boxed{Q_e = \frac{R_t}{\omega_0 L} = \omega_0 C R_t}$$

$$\rightarrow \text{Gain} = \frac{V_o}{V_{in}}$$

$$\& \boxed{V_o = -g_m V_{be} \cdot Z}$$

$$\text{where } Z = R_t \parallel j\omega L \parallel \frac{1}{j\omega C}$$

$$\Rightarrow Y = \frac{1}{Z} = \frac{1}{R_t} + \frac{1}{j\omega L} + j\omega C$$

$$= \frac{1}{R_t} \left[ 1 + \frac{R_t}{j\omega L} + j\omega C R_t \right]$$

$$= \frac{1}{R_t} \left[ 1 + \frac{R_t}{j\omega_0 L} \left( \frac{\omega_0}{\omega} \right) + j\omega_0 C R_t \left( \frac{\omega}{\omega_0} \right) \right]$$

$$\Rightarrow Y = \frac{1}{R_t} \left[ 1 + \frac{Q_e}{j} \left( \frac{\omega_0}{\omega} \right) + j Q_e \left( \frac{\omega}{\omega_0} \right) \right]$$

$$\Rightarrow Y = \frac{\left[ 1 + j Q_e \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right]}{R_t}$$

$$\Rightarrow \boxed{Z = \frac{1}{Y} = \frac{R_t}{\left[ 1 + j Q_e \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right]}}$$

→ Let. ' $\delta$ ' indicates the fractional frequency variation i.e., variation in frequency expressed as a fraction of the resonant frequency

$$\Rightarrow \delta = \frac{\omega - \omega_0}{\omega_0} = \frac{\omega}{\omega_0} - 1$$

$$\Rightarrow \frac{\omega}{\omega_0} = \delta + 1$$

$$\rightarrow Z = \frac{R_L}{[1 + jQ_L(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega})]} = \frac{R_L}{[1 + jQ_L(\delta + 1 - \frac{1}{\delta + 1})]}$$

$$\Rightarrow Z = \frac{R_L}{1 + jQ_L(\frac{\delta^2 + 2\delta}{\delta + 1})}$$

$$\Rightarrow \boxed{Z = \frac{R_L}{1 + j2\delta Q_L \left[ \frac{\delta/2 + 1}{\delta + 1} \right]}}$$

→ If  $\omega$  is close to ' $\omega_0$ '

$$\delta \ll 1 \Rightarrow \boxed{Z = \frac{R_L}{1 + j2\delta Q_L}}$$

→ If  $\omega = \omega_0 \Rightarrow \delta = 0$ .

$$\Rightarrow \boxed{Z = R_L}$$

→ We know  $R_p = \frac{\omega^2 L^2}{R}$

and at resonance  $X_L = X_C \Rightarrow \omega L = \frac{1}{\omega C}$ .

$$\Rightarrow \omega^2 = \frac{1}{LC}$$




$$\Rightarrow R_p = \frac{L^2}{LCR} = \frac{L}{RC}$$

$$\rightarrow Q_0 = \frac{\omega_0 L}{R}$$

$$\Rightarrow R_p = \frac{\omega_0^2 L^2}{R} = Q_0^2 \cdot R = \omega_0 L Q_0$$

↓

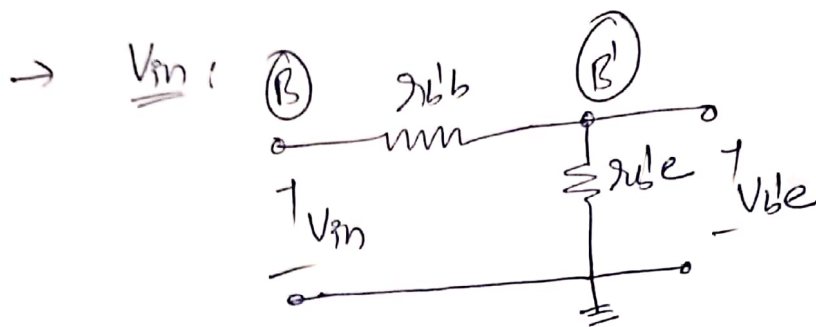$\rightarrow \because R_p = Q_0^2 \cdot R \Rightarrow Q$ -factor is also known as circuit magnification factor.



$$\Rightarrow V_{be} = V_m \cdot \frac{r_{ie}}{r_{ib} + r_{ie}}$$

$$\Rightarrow V_m = \frac{V_{be} \cdot (r_{ib} + r_{ie})}{r_{ie}}$$

$$\rightarrow A_v = \frac{V_o}{V_m} = \frac{-g_m V_{be} \cdot Z}{V_{be} \cdot \frac{(r_{ib} + r_{ie})}{r_{ie}}}$$

$$\Rightarrow A_v = -g_m \left[ \frac{r_{ie}}{r_{ie} + r_{ib}} \right] \cdot Z$$

$$\Rightarrow A_v = -g_m \left[ \frac{r_{ie}}{r_{ie} + r_{ib}} \right] \left[ \frac{R_t}{1 + j 2 \delta Q_e} \right]$$

→ At resonance  $\delta = 0$

$$\Rightarrow (A_v)_{\text{resonance}} = \frac{-g_{m1} R_t}{(g_{s1} + g_{s2})} \leftarrow \text{Max. gain}$$

$$\Rightarrow \left[ \frac{A_v}{(A_v)_{\text{resonance}}} = \frac{1}{1 + j2\delta Q_e} \right]$$

$$\Rightarrow \left| \frac{(A_v)}{(A_v)_{\text{resonance}}} \right| = \frac{1}{\sqrt{1 + (2\delta Q_e)^2}}$$

$$\delta \phi = -\tan^{-1}(2\delta Q_e)$$

→ At frequency ' $\omega_1$ ' below the resonant frequency

$$\text{let } \delta = -\frac{1}{2Q_e}$$

$$\Rightarrow \left| \frac{A_v}{(A_v)_{\text{resonance}}} \right| = \frac{1}{\sqrt{2}} = 0.707$$

$$\delta (A_v)_{\text{dB}} = (A_{v\text{resonance}})_{\text{dB}} - 3\text{dB}$$

∴ The frequency ' $\omega_1$ ' is the lower '3dB' frequency.

→ Similarly at frequency ' $\omega_2$ ' above ' $\omega_0$ ' let

$$\delta = \frac{1}{2Q_e}$$

$$\Rightarrow \left| \frac{A_v}{A_{v\text{resonance}}} \right| = \frac{1}{\sqrt{2}} = 0.707$$

Hence frequency ' $\omega_2$ ' is the upper '3dB' frequency.

$$[A_{v\text{dB}} = (A_{v\text{resonance}})_{\text{dB}} - 3\text{dB}]$$

→ Bandwidth

$$BW = \omega_2 - \omega_1$$

$$= \left[ \frac{(\omega_2 - \omega_0) + (\omega_0 - \omega_1)}{\omega_0} \right] \times \omega_0$$

$$\Rightarrow BW = \left[ \left( \frac{\omega_2 - \omega_0}{\omega_0} \right) + \left( \frac{\omega_0 - \omega_1}{\omega_0} \right) \right] \omega_0$$

$$= (\delta + \delta) \omega_0$$


$$\Rightarrow \boxed{BW = 2\delta \omega_0}$$

$$\rightarrow \text{But } \delta = \frac{1}{2Q_e} \Rightarrow \boxed{BW = \frac{\omega_0}{Q_e}} = \frac{\omega_0}{\omega_0 R_t C} = \frac{1}{C R_t}$$

$$= \frac{\omega_0 \omega_0 L}{R_t} = \frac{\omega_0^2 L}{R_t}$$

$$\Rightarrow \boxed{BW = 2\delta \omega_0 = \frac{\omega_0}{Q_e} = \frac{1}{C R_t} = \frac{\omega_0^2 L}{R_t}}$$

→ Frequency Response -

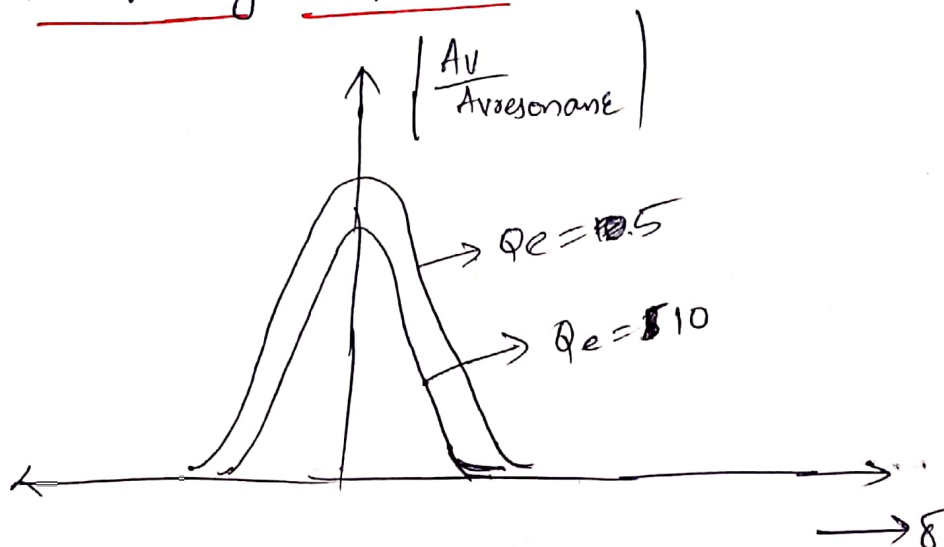

Frequency Response .

→ Effect of Cascading single tuned Amplifiers on Bandwidth :-

→ Relative gain  $\left[ \frac{A}{A_{\text{resonance}}} \right] = \frac{1}{1 + j2\delta Q_e}$  for single stage

→ For 'n' stages

$$\left[ \frac{A}{A_{\text{resonance}}} \right]^n = \left[ \frac{1}{1 + j2\delta Q_e} \right]^n$$

$$\Rightarrow \left| \frac{A}{A_{\text{res.}}} \right|^n = \left[ \frac{1}{\sqrt{1 + (2\delta Q_e)^2}} \right]^n = \frac{1}{\sqrt{2}}$$

$$\Rightarrow 1 + (2\delta Q_e)^2 = 2^{1/n}$$

$$\Rightarrow 2\delta Q_e = \pm \sqrt{2^{1/n} - 1}$$

$$\Rightarrow \delta = \pm \frac{1}{2Q_e} \sqrt{2^{1/n} - 1}$$

$$\delta = \frac{\omega - \omega_0}{\omega_0} = \frac{f - f_0}{f_0}$$

$$\Rightarrow (f - f_0) = \pm \frac{f_0}{2Q_e} \sqrt{2^{1/n} - 1} \quad ; \quad \begin{matrix} + \rightarrow f_H \\ - \rightarrow f_L \end{matrix}$$

$$\Rightarrow (f_H - f_0) = \frac{f_0}{2Q_e} \sqrt{2^{1/n} - 1}$$

$$\Rightarrow (f_L - f_0) = -\frac{f_0}{2Q_e} \sqrt{2^{1/n} - 1}$$

$$\Rightarrow f_0 - f_L = \frac{f_0}{2Q_e} \sqrt{2^{1/n} - 1}$$

$$\begin{aligned}
 \rightarrow (BW)_{\text{overall}} &= f_H - f_L \\
 &= (f_H - f_0) + (f_0 - f_L) \\
 &= \frac{f_0}{Q_e} \sqrt{2^{V_n} - 1}
 \end{aligned}$$

$$\Rightarrow \boxed{(BW)_{\text{overall}} = BW_1 \sqrt{2^{V_n} - 1}} \quad \leftarrow \text{Bandwidth for } n\text{-stages}$$

Where  $BW_1 = \frac{f_0}{Q_e} \rightarrow$  Bandwidth for single stage.

$$\begin{aligned}
 \rightarrow \text{let } n=2 &\Rightarrow (BW)_{\text{overall}} = BW_1 \sqrt{2^{V_2} - 1} \\
 &= BW_1 \times 0.643.
 \end{aligned}$$

$$\begin{aligned}
 n=3 &\Rightarrow (BW)_{\text{overall}} = BW_1 \sqrt{2^{V_3} - 1} \\
 &= BW_1 \times 0.509.
 \end{aligned}$$


### → Stagger Tuned Amplifiers :-

- Stagger tuned amplifiers use a no. of single tuned stages in cascade, the successive tuned circuits being tuned to slightly different frequencies.

→ let in a stagger tuned circuit, 2 single tuned cascade amplifiers having a certain bandwidth are taken.

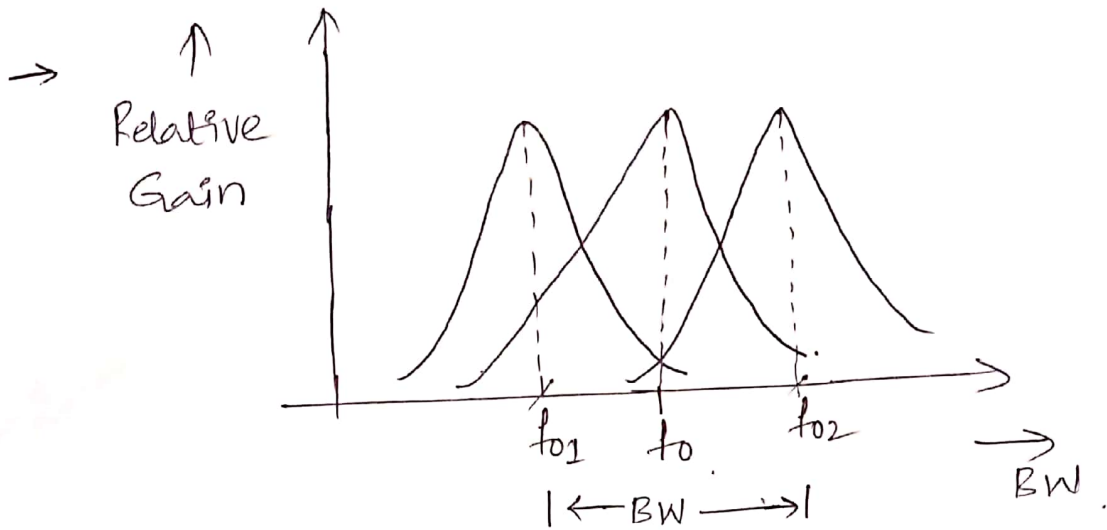→ The resonant frequencies of the two tuned circuits are adjusted such that they are separated by an amount equal to Bandwidth of each stage.





Conditions

$$1. f_{02} - f_{01} = BW.$$

$$2. BW_{\text{stagger}} = \sqrt{2} BW.$$

$$\rightarrow \frac{A}{A_{res}} = \frac{1}{1 + j2\delta Qe}$$

$$\text{let } x = 2\delta Qe.$$

$$\text{then } \frac{A}{A_{res}} = \frac{1}{1 + jx}, \text{ At } 3\text{dB } \delta = \frac{1}{2Qe}$$

$$\boxed{BW = \frac{f_0}{Qe} = 2\delta f_0.}$$

$$\rightarrow \left[ \frac{A}{A_{res}} \right]_1 = \frac{1}{1 + j(x-1)}, \quad \left[ \frac{A}{A_{res}} \right]_2 = \frac{1}{1 + j(x+1)}$$

$$\Rightarrow \left[ \frac{A}{A_{res}} \right]_{\text{stagger}} = \left[ \frac{A}{A_{res}} \right]_1 \left[ \frac{A}{A_{res}} \right]_2$$

$$\Rightarrow \left[ \frac{A}{A_{res}} \right]_{\text{stagger}} = \frac{1}{2 - x^2 + 2jx}$$

$$\Rightarrow \left| \frac{A}{A_{res}} \right|_{\text{stagger}} = \frac{1}{2\sqrt{1 + 4\delta^4 Qe^4}}$$